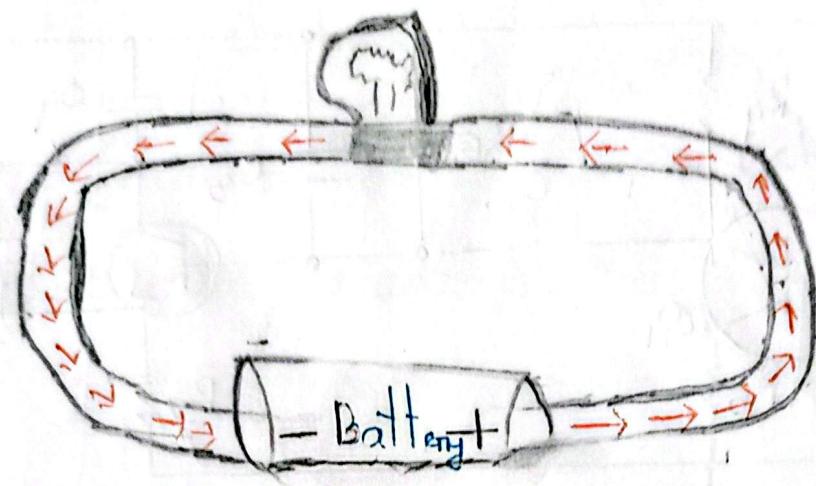


Dc Circuits - Basic Concepts

Date




An electric circuit is a closed path through which electric current flows.


■ interconnection of electrical elements.

AS like,

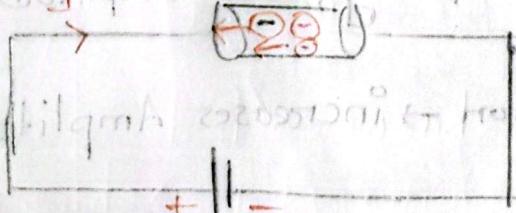Battery + Wires + Switch + Bulb → connected together
= Electric circuit.



Date :

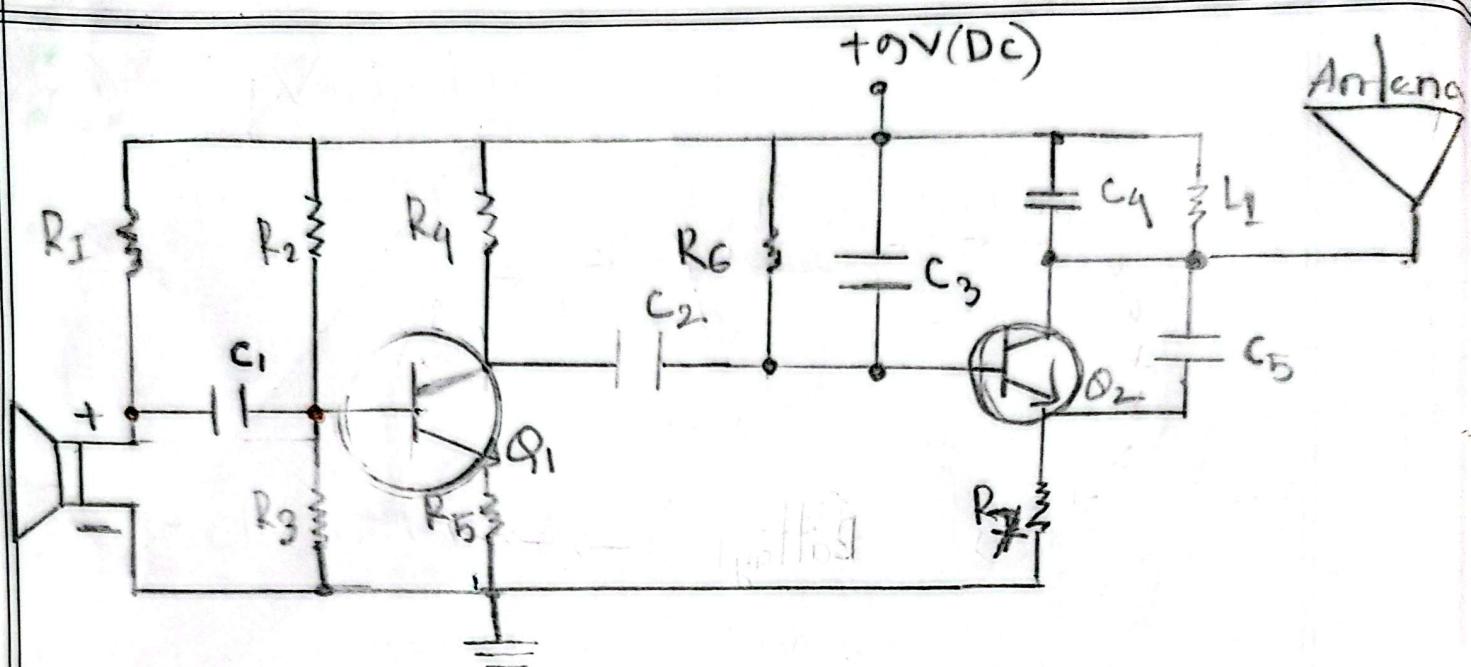

Electric circuit of radio transmitter

Summary :-

Sound wave \rightarrow (voice \rightarrow has Amplitude + Frequency)

Microphone \rightarrow (Converts Sound into voltage Signal
Frequency Unchanged) \rightarrow Amplitude Strong

Electrical Signal \rightarrow (Same Frequency, low amplitude)

Amplifier \rightarrow (Transistor \rightarrow increases Amplitude, Frequency)

Strong electrical sig. \rightarrow (Same Frequency, high Amplitude)

REDMI NOTE 13
Antenna
SHAKIB HOSSAN
 \rightarrow (Transmits into air) The antenna
takes Strong Signal and sent to Space.)

Date:

Problem 1: How much charge is represented by 4600 electrons? (Answer is 7.368 × 10⁻¹⁶ C)

$$Q = (\text{number of electrons}) \times (\text{charge of one electron})$$

$$Q = 4600 \times 1.602 \times 10^{-19} =$$

$$= 7.368 \times 10^{-16} \text{ C}$$

$$(F_R)_{\text{loss}} + (F_R)_{\text{bias}} = \sqrt{U_1 + U_2} = (F_R)$$

problem 2: calculate the amount of charge represented by six million protons.

$$Q = N \times q$$

$$= (6 \times 10^6) \times (1.602 \times 10^{-19})$$

$$= 9.61 \times 10^{-13} \text{ C}$$

problem 3: The total charge entering a terminal is given by $q = 5t \sin 4\pi t \text{ mC}$. Calculate the current $I = 0.5s$.

Alternative:

$$q = 6t \sin 8\pi t \text{ mC}$$

$$I = 2.5$$

SHAKID HOSSAN

Date

Solution: $i = \sin(kt)$ with $k = 4\pi$

$$i = \frac{di}{dt} = \frac{d}{dt} (5 \cdot \sin(4\pi t))$$

$$U = 5t$$

$$U' = 5$$

$$\begin{aligned}V &= \sin(4\pi t) \\V' &= \cos(4\pi t) \cdot \frac{d(4\pi t)}{dt} \\V' &= \cos(4\pi t) \cdot 4\pi \\V' &= 4\pi \cos(4\pi t)\end{aligned}$$

chain Rule

$$S(t) = \sin(kt)$$

$$S'(t) = k \cos(kt)$$

$$\frac{d}{dt} [\sin(u)]$$

$$= \cos(u) \cdot \frac{du}{dt}$$

$$u = 4\pi t$$

$$i(t) = UV + U'V = 5 \cdot \sin(4\pi t) + 5 \cdot (4\pi \cos(4\pi t))$$

$$= 5 \cdot \sin(4\pi t) + 20\pi \cos(4\pi t)$$

for $t = 0.5$

$$\begin{aligned}i(0.5) &= 5 \cdot \sin(4\pi \times 0.5) + 5 \times 0.5 \cdot (4\pi \cos(4\pi \times 0.5)) \\&= 5 \cdot \sin(4\pi \times 0.5) + 20\pi \times 0.5 \cos(4\pi \times 0.5) \\&= 5 \cdot \underline{\sin(2\pi)} + \underline{20\pi \times 0.5 \cos 2\pi} \\&= 5 \times 0 + 20\pi \times 0.5 \times 1\end{aligned}$$

$$4\pi \times 0.5 = 2\pi$$

$$\sin 2\pi = 0$$

$$\cos 2\pi = 1$$

Date :

$$q(t) = 6t \sin(8\pi t)$$

$$i(t) = \frac{dq}{dt}$$

$$U = 6t, \quad U' = \frac{du}{dt} = 6,$$

$$V = \sin(8\pi t); \quad V' = \frac{dv}{dt} = 8\pi \cos(8\pi t)$$

$$i(t) = U'V + UV' = 6 \times \sin(8\pi t) + 6t \times 8\pi \cos(8\pi t)$$

$$i(t) = 6 \sin(8\pi t) + 48\pi t \cos(8\pi t)$$

when $t = 2.5$

$$i(2.5) = 6 \sin(8\pi \times 2.5) + 48\pi \times 2.5 \cos(8\pi \times 2.5)$$

$$= 6 \sin(20\pi) + 48\pi \times 2.5 \cos(20\pi)$$

$$= 6(0) + 48\pi(2.5) \times 1(-1) = -$$

$$= 120\pi \text{ mA} = 376.8 \text{ mA.}$$

IS in example 2. $q = (10 - 10e^{-2t}) \text{ mC}, t = 1.0 \text{ s.}$

$$q(t) = (10 - 10e^{-2t}) \text{ mC}$$

$$i(t) = \frac{dq}{dt} \quad t = 1 \text{ s.}$$

$$U = -10, \quad U' \frac{du}{dt} = 0$$

$$i(t) = U'V + UV' = 0 + [0 \cdot e^{-2t} + (-10)(-2e^{-2t})] V = e^{-2t}, \quad \frac{dv}{dt} = -2e^{-2t}$$

$$= 20e^{-2t}$$

$$t = 1, \quad i(1) = 20e^{-2(1)} = 20e^{-2}$$

REDMI NOTE 13

$$\bar{I} = 2.0 \times 0.1353 = 2.706 \text{ mA.}$$

Date:

Determine the total charge entering (1) A terminal between $t=1s$, and $t_2=2s$ if the current passing the terminal is $i = (3t^2-1)A$.

$$i(t) = (3t^2 - 1) A$$

$$\text{we know, } q = \int_{t_1}^{t_2} i(t) dt$$

$$q = \int_1^2 (3t^2 - 1) dt$$

$$\int Kdt = Kt + C$$

$$= \left[\left(t^3 \right) - \left(\frac{t^2}{2} \right) \right]_1^2$$

$$q = t^3 - \frac{t^2}{2}$$

$$= \left(2^3 - \frac{2^2}{2} \right) - \left(1^3 - \frac{1^2}{2} \right)$$

$$= (8 - 2) - (1 - 0.5) = 5.5$$

$$= 5.5 \text{ Amperes}$$

$$= 5.5 \text{ C}$$

$$= 5.5 \text{ Coulombs}$$

The current flowing through an element is

$$\int_0^t i(t) dt$$

so to calculate total charge entering the element from $t = 0$ to $t = 25$,

$$q = \int_0^1 i(t) dt$$

$$q = \int_0^1 4dt + \int_1^2 4t^2 dt$$

$$\begin{aligned} q &= 4 \times \int_0^1 t^2 + 4 \int_1^2 t^2 dt \\ &= 4 + 4 \left[\frac{t^3}{3} \right]_1^2 \\ &= 4 + 4 \left[\frac{1^3}{3} - \frac{1^3}{3} \right] \end{aligned}$$

$$\begin{aligned} q &= 4 + 4 \cdot \frac{2^3 - 1^3}{3} \\ &= 4 + 4 \cdot \frac{8 - 1}{3} \\ &= 4 + 4 \cdot \frac{7}{3} \\ &= 4 + 9.333 \end{aligned}$$

$$= 13.333 C$$

Voltage.

Dc and ac current.


Date.....

D^orect current is a type of electric current that shows in one direction only and doesn't change over time.

DC



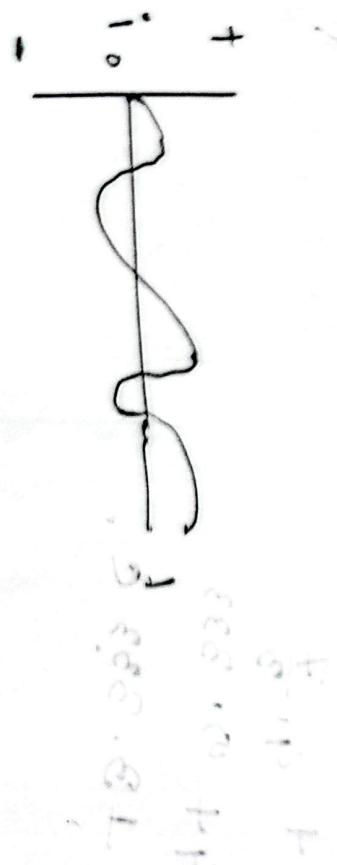Ac current is a type of current that changes direction and strength over time.




Voltage :

Date...../...../.....

Is the voltage and current usually non-constant?

Ans: No

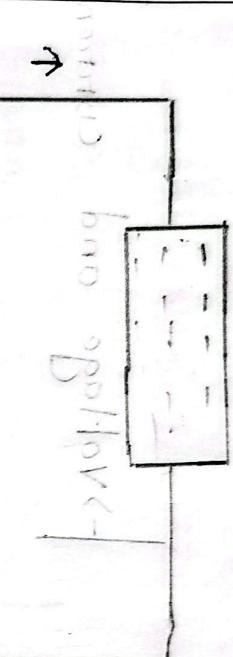

Voltage is the amount of energy required to move one coulomb of charge from one point to another.

High potential is below potential


Dimensional formula $J = \text{newton meter/coulomb}$

$$V = \frac{\omega}{q}, \quad q = i \times t, \quad \rightarrow \omega = \text{energy of work,}$$

Dimension of ω is $J \cdot m^2 \cdot s^{-2}$

Dimension of i is $A \cdot s^{-1}$

Dimension of t is s

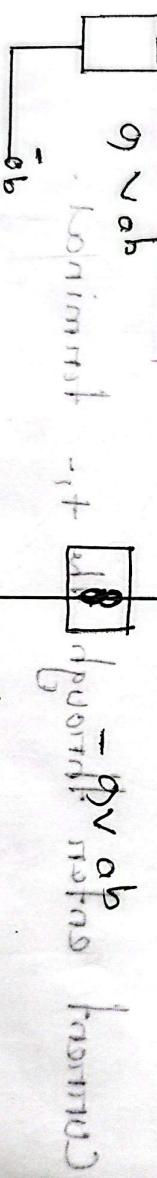

Polarity of voltage.

Voltage Value	Meaning
$V_{ab} = +5V$	a is higher than b
$V_{ab} = -5V$	a is lower than b

Power of energy.

Date: 20/11/2022

Power in power measures how fast energy is used in a circuit.

1. Instantaneous power
in form of current
more simply $P = V \times I$
form of time


$$P = \frac{W}{t}$$

→ How fast energy is used or consumed.

Notation $W = P \times t$ also \rightarrow Energy consumed.

2. Signs of power:
Positive power → element is absorbing → Resistor,
Negative power → element is supplying battery.

Current enters through +, - terminal.

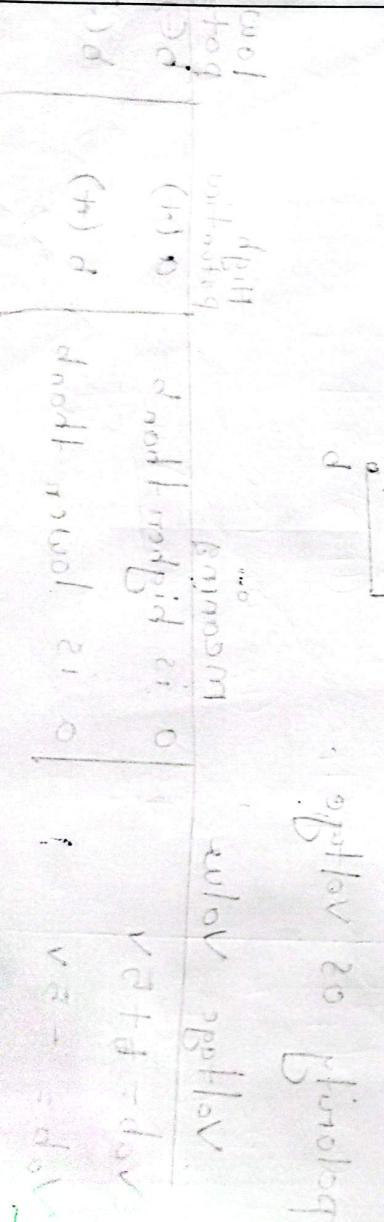

problem Solved.

Date

- Ques. An energy source with constant current of 2A passes through 10 light bulbs. If 2.3 kJ is given off in the form of light and heat energy calculate the voltage drop across the bulbs.

Given,

$$I = 2\text{A}$$

$$T = 10\text{s}$$

$$W = 2.3\text{ kJ} = 2300\text{ J}$$

$$\left| \begin{array}{l} \text{pd} \\ \text{pd} = (10) \end{array} \right.$$

$$Q = I \cdot T$$

$$Q = 2 \times 10 = 20 \text{ coulombs}$$

$$i_C = V$$

$$V = \frac{W}{Q} = \frac{2300}{20} = 115 \text{ V}$$

$$V = 115 \sqrt{10} \text{ V}$$

To move charge from point a to point b requires

- 30 J . Find the voltage drop V_{ab} (a) $q = 6\text{C}$, (b) $q = -3\text{C}$.

$$W = -30\text{ J}$$

$$(a) q = 6\text{C}, (b) q = -3\text{C}$$

$$(1000)^{200} \div (1)$$

$$(a) \sqrt{\frac{W}{q}} = \frac{-30}{(6000)^{200}} = -\frac{1}{(1000)^{200}} \text{ J}^{-1}$$

$$(b) \sqrt{\frac{W}{q}} = \frac{-30}{(-3000)^{200}} = -\frac{1}{(1000)^{200}} \text{ J}^{-1}$$

$$\sqrt{\frac{W}{q}} = \frac{-30}{(-3000)^{200}} = -\frac{1}{(1000)^{200}} \text{ J}^{-1}$$

Date.....

~~Find the power delivered to an element at $t = 9 \text{ ms}$ if the current entering its positive terminal is $i = 5 \cos(60\pi t) \text{ A}$ and the voltage is (a) $V = 3i$, (b) $V = 3 \frac{di}{dt}$.~~

Ans

(a)

$$I \cdot V = P$$

$$(a \cos \theta)$$

$$\Delta \varphi = \theta$$

$$20L = r$$

$$L_{50\Omega} = 14.2 \text{ ms}$$

$$- (ab)^2 = a^2 b^2$$

$$\begin{aligned} V &= 3i \\ V &= \sqrt{X_1^2 + X_2^2} \\ &= \sqrt{3^2 + 3^2} \\ &= 3(\sqrt{\cos^2(\theta) + \sin^2(\theta)}) \\ &= 3(\sqrt{\cos^2(60\pi t) + \sin^2(60\pi t)}) \\ &= 3(\sqrt{1}) \\ &= 3 \text{ V} \end{aligned}$$

$$= 45 \cos^2(60\pi t) \text{ V. Radians from 0 to } 2\pi \text{ rad.}$$

$$P = 0.003 \text{ Jov point}$$

$$P = 45 \cos^2(60\pi \times 3 \times 10^{-3}) \text{ W} = 45 \cos^2(0.18\pi) = 53.048 \text{ W.}$$

(b) Given,

$$i(t) = 5 \cos(60\pi t)$$

$$i = P \quad (d)$$

$$\frac{di}{dt} = V$$

$$\frac{d}{dt} [\cos(60\pi t)] = -\sin(60\pi t) \times \frac{d}{dt}(60\pi t) = -60\pi \sin(60\pi t)$$

$$= -5(60\pi) \sin(60\pi t)$$

$$\frac{di}{dt} = -300\pi \sin(60\pi t)$$

$$= \frac{V}{R} = \frac{W}{P}$$

Date :

$$V = 3,$$

$$V = 3 \times (-306\pi \sin(60\pi t))$$

$$= -918\pi \sin(60\pi t)$$

$$t = 0.063,$$

$$V = -918\pi \times 0.5360 = -1515.0 \text{ V}$$

$$I = 4.2215 A$$

$$P = V \times I$$

$$= (-1515.0) \times (4.2215)$$

$$= -6375.9 \text{ W} \quad \text{or} \quad 6375.9 \text{ W}$$

$$(+) \cdot 5 \cos(60\pi t)$$

~~• Radian and degree
EE. E.S.V.
Voltage Ac form
Radian not
sinusoidal degree~~

How much energy does a 100W electric bulb consume in two hours.

$$W = Pt = 100(W) \times 60(\text{min}) \times 60(s/\text{min})$$

$$= 720,000 \text{ J} = 720 \text{ kJ}$$

$$W = Pt = 100W \times 2h = 200 \text{ Wh}$$

Find the power delivered into the element

Example 15. If $I = 5 \text{ m.s}^{-1}$ is the current through the same but the voltage is: a) $V = 21$

$$(b) V = (10 + 5 \sin(60\pi t))$$

(a) we know $P = V^o$,

$$V = 2 \text{ (i)}$$

$$= 2 \text{ (i)}^2$$

$$= 50 \cos^2(60\pi t)$$

$$= 50 \cos^2(60\pi t) \cdot 0.2151 = 0.2050 \times 5000 = V$$

$$(15 - t) = 0.005t;$$

$$= 50 \cos^2(60\pi \times 0.005)$$

$$\approx 17.27 \text{ W}$$

$$(b) i^o(t) = 5 \cos^2(60\pi t), \quad t = 0.005 \text{ s} \Rightarrow 0.2050 =$$

$$\sqrt{A} = 10 + 5\sqrt{2} \text{ A}$$

$$\int_0^t idt = 5 \cos(60\pi t) dt$$

$$\int_0^{0.005} 5 \cos(60\pi t) dt = 5 \cdot \frac{1}{60\pi} \sin(60\pi t) \Big|_0^{0.005} =$$

$$= \frac{1}{12\pi} \sin(60\pi \cdot 0.005) = \frac{1}{12\pi} \times 0.001 = 1.9 \times 10^{-5} = 1.9 \text{ C}$$

$$\therefore \int_0^t idt = \frac{5}{12} \sin(60\pi t)$$

$$\text{from left } \frac{5}{12} \sin(60\pi \times 0.005) = \text{left hand side}$$

$$\text{current } I = 5 \cos(60\pi t) \text{ A}$$

$$= 5 \cos(60\pi \cdot 0.005) = 5 \cos(0.314) = 2.03$$

$$N = \frac{1}{2} \times 200 = 100$$

$$C = V$$

$$(100) \text{ mA R} 0.005 \rightarrow X \Omega = 4$$

$$(100) \text{ mA R} 0.005 \rightarrow 2$$

$$\boxed{\text{Shift} + \text{Menu} + 2 \text{ Ang} + 2 \text{ Radian} \times \checkmark}$$

$$(21.55, 1) \times (0, 21.51) =$$

$$\boxed{A = 21.55, \Delta = 1^\circ}$$

Date: 11/10/2023

A Slope element ~~25 ohms~~ when connected to 240V line. How long does it takes to consume 180 kJ

$$t = \frac{180,000}{180 \times 15}$$

$$180,000 \text{ J} = 180 \times 15 \text{ W}$$

$$\frac{180,000}{3600} = 50 \text{ s}$$

$$P = \sqrt{V}$$


$$t = \frac{W}{P} = \frac{W}{\sqrt{V}}$$

Answe: ~~180,000 J / 180 W = 1000 s~~

Answe: ~~180,000 J / 180 W = 1000 s~~

Answe: ~~180,000 J / 180 W = 1000 s~~

Answe: ~~180,000 J / 180 W = 1000 s~~

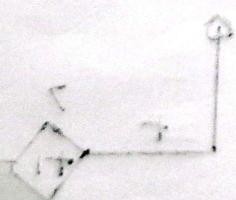

Bottom method

Answe:

REDMI NOTE 13
SHAKIB HOSSAN

Circuit Elements

Date

Two types

Dependent and Independent

Passive


They cannot produce energy only store it.

Active

Supply energy
Generation Batt


Ideal Independent:

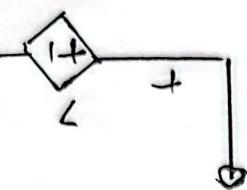This is a special active element gives final voltage or current that depend on other part circuit provides specified constant voltage or current.




Dependent voltage e

Depends on Another voltage or current.

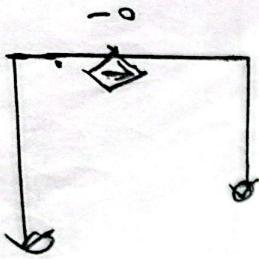

Dependent current source.

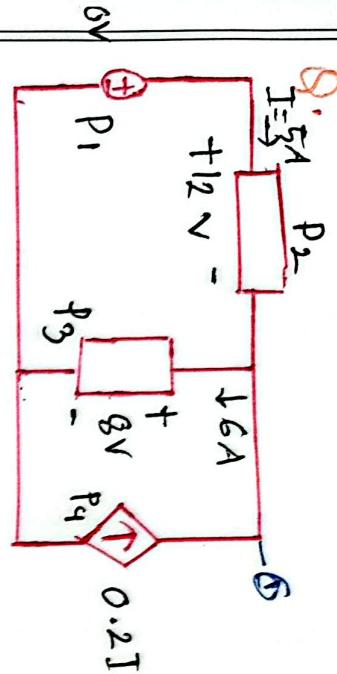

Q calculate the power supplied on absorbed by each element

Solution:


$$P_1 = 20(-5) = -100 \text{ W} \text{ (supplied)}$$

$$P_2 = 12 \times 5 = 60 \text{ W} \text{ (Absorbed)}$$

$$P_3 = 8 \times 6 = 48 \text{ W} \text{ (Absorbed)}$$

$$P_4 = 8 \times (-1) = -8 \text{ W} \text{ supplied.}$$

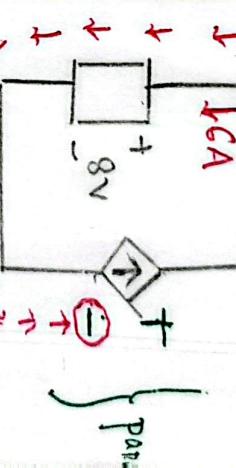④ Voltage is always measured between two points.



⑤ Two element can have same pair of terminals. They will have same voltage.


$$\therefore P_1 + P_2 + P_3 + P_4 = -100 + 60 + 48 - 8$$

$$= 0$$

Total power Supplied = Total power absorbed
(+ Power absorbed) + (-Power supplied) = 0

Nothing is lost or created - it only moves from one element to another.

Date

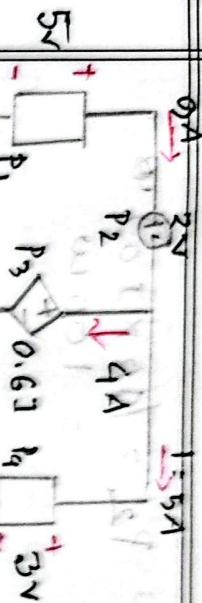

$$P_1 = 5 \times (-6) = -30W$$

$$P_2 = 2 \times 6 = +12W$$


$$P_3 = 3 \times 4 = 12W$$

$$P_4 = 3 \times 6 = 18W$$

* Compute the power absorbed or supplied by each component of a circuit (except source)

$$\text{Ans} (i) P_1 = 5 \times (-6) = -30W$$
$$(ii) P_2 = 2 \times 6 = +12W$$
$$(iii) P_3 = 3 \times 4 = 12W$$
$$(iv) P_4 = 3 \times 6 = 18W$$

1.18:

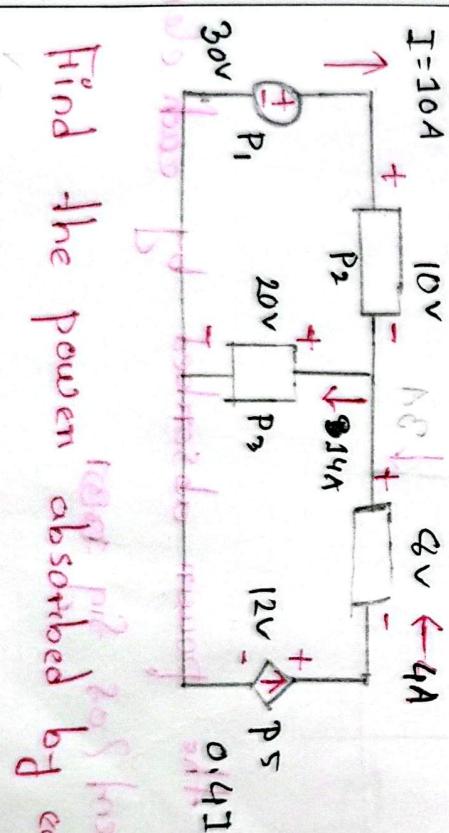

Find the power absorbed by each of the elements.

Date

Solution:

$$P_1 = 30 \times (-10) \text{ wats}$$

$$P_2 = (10 \times 10) \text{ wats}$$

$$= 100 \text{ w}$$

$$P_3 = (4 \times 20)$$


$$= 280 \text{ w}$$

$$P_5 = (0.4) \times 12$$

$$= 4.8 \times (0.4 \times -10)$$

$$= 12 \times (-4)$$

$$\approx -48 \text{ w}$$

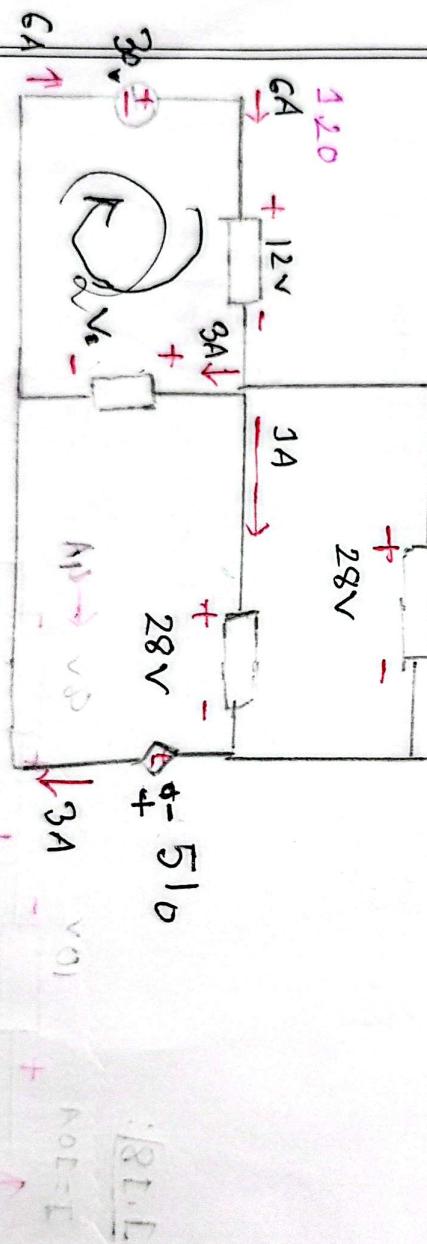

$$W_S = P \times t = 100 \times 10 = 1000 \text{ J}$$

$$W_S = P \times t = 100 \times 10 = 1000 \text{ J}$$

$$W_S = P \times t = 100 \times 10 = 1000 \text{ J}$$

$$12V + 18V = 30V$$

REDMI NOTE 13
SHAKIB HOSSAN

Find V_o and the power absorbed by each element in the current? pos sig \rightarrow downwards

$$V_o = 18V + 30V - 12V$$

$$= 36V$$

1/V
1/A

Date

$$P_{3a} = 30 \times (-6) = -180 \text{ W}$$

$$P_{12} = 12 \times 6 = 72 \text{ W}$$

$$P_{28} = 28 \times 1 = 28 \text{ W}$$

$$P_{45} = 10 \times (-3) = -30 \text{ W}$$

$$\boxed{V_x = K \times I_{control}}$$

V_x = dependent voltage source
Voltage

I control = The controlling current (from another branch)
k = proportionally constant.

We know,

Power
balance

$$= P_1 + P_2 + P_3 + P_4 + P_5 + P_6 + P_7 = 0$$

$$\Rightarrow -180 + 72 + 28 + 56 + 28 - 30 = 0$$

$$\Rightarrow 0 \times 0 = 210 - 156$$

$$\Rightarrow 0 \times 0 = 54$$

$$= 0 = 18V$$

$$\begin{cases} V = 5I_0 \\ I_0 = 2A \end{cases}$$

$$\begin{cases} V = 5 \times 2 = 10V \\ \end{cases}$$

$$\begin{cases} k = 5 \\ I_0 = 2A \end{cases}$$

$$\begin{cases} P_0 = V_0 I_0 \\ V_0 = \frac{P_0}{I_0} \end{cases}$$

$$\sum P = 0$$

Ohms law

Date

Resistance: opposes the flow of electric current.

$$R = \rho \frac{L}{A}$$

length
Area
Resistivity

Ohms law: Voltage is directly proportional to current

$$V = i R$$

Voltage
Current

$$R = \frac{V}{I}$$

$$1\Omega = 1 V/A$$

conductance:-

How easily current flows through a material

R is low \rightarrow high conductance

R is high \rightarrow low conductance


$$G_1 = \frac{1}{R}$$

mho u


$$I = G_1 V$$

$$P = V_1^2 = I^2 R = \frac{V^2}{R}$$
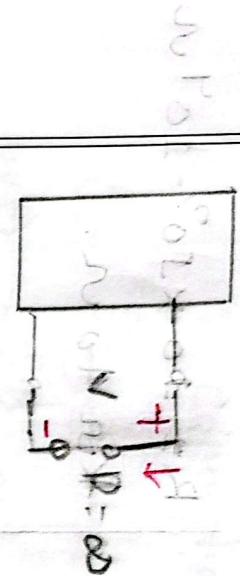
$$P = V_1^2 = I^2 G_1 = \frac{V^2}{G_1}$$



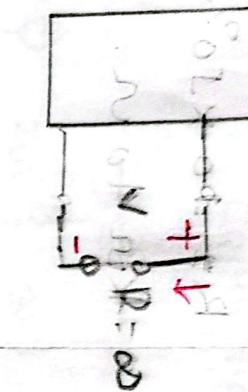
Higher potential to a lower potential = $V - IR$



$$V = \lim_{R \rightarrow \infty} V_{out}$$

Low Potential to a higher potential $\propto \frac{1}{R}$.

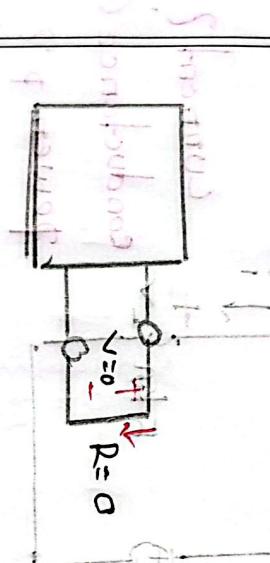
Open circuit resistance approaching infinity



Circuit + very low to zero, almost no voltage drop. Current = $I = \frac{V}{R} \rightarrow$ extremely large.

Short circuit resistance approaching zero
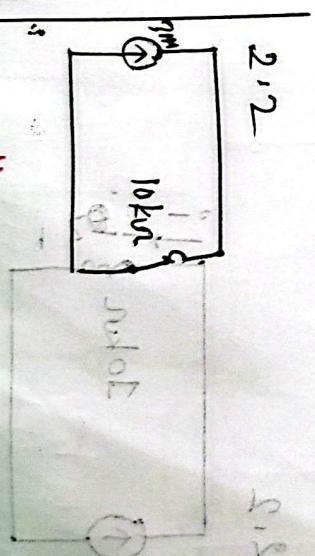
$$2A \quad R = \frac{V}{I} = \frac{120}{2} = 60 \Omega$$



2.1:

$$I = \frac{V}{R}$$

$$= \frac{110}{15}$$

$$I = 7.33A$$

p. 2

Date

Voltage of 1 ohm's conductance

Voltage of 10¹⁰ sec conduction
 $\sqrt{I_P} \Rightarrow \text{Initial conduction} = \frac{1}{R}$

$$R = 10 \times 10^3 = 10^4 \Omega$$

$\frac{1}{104} \times 100 = 9.6\%$

Digitized by srujanika@gmail.com

11
36 x 3x10

Chemical reaction on board
of $\text{Na}_2\text{O} + \text{H}_2\text{O} \rightarrow \text{NaOH}$

Current?
conductance G_1 ?
power p?

A hand-drawn circuit diagram consisting of a rectangle representing a closed switch. Inside the rectangle, there is a battery symbol with a voltage value of "6V" written next to it. A resistor symbol with a value of "5kΩ" is also present inside the rectangle. The entire circuit is enclosed in a rectangular loop.

$$\text{Solve for } I \text{ in } I = \frac{V}{R} = \frac{30}{5 \times 10^3} = 6.0 \text{ mA}$$

$$I = \frac{V}{R} = \frac{30}{5 \times 10^3} = 6 \text{ mA}$$

$$\begin{array}{r} P \\ - L \\ \hline 10 \\ 11 \\ \hline 30 \\ 6 \times 10 \\ \hline 180 \end{array}$$

$$\phi = \frac{1}{2} R = (6 \times 10^2)^2 \pi \times 10^3 = 180 \text{ rad}$$

$$P = \sqrt{2} G_1 = (35) 0.2 \times 10^3 = 180 \text{ mW}$$

Voltage? conductance? power p?


✓ spot for 3d. photos (60)

she has a snowshoe

Date


Branches: A Branch represent a single element

Such as . Voltage Sources . resistance

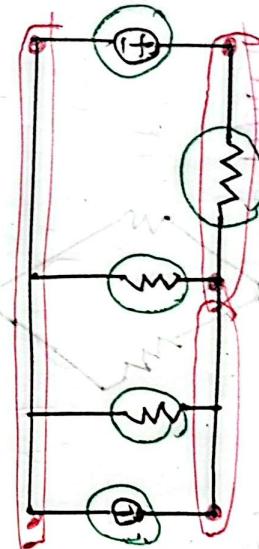

3 branch


Loop : a loop is any closed path in a circuit

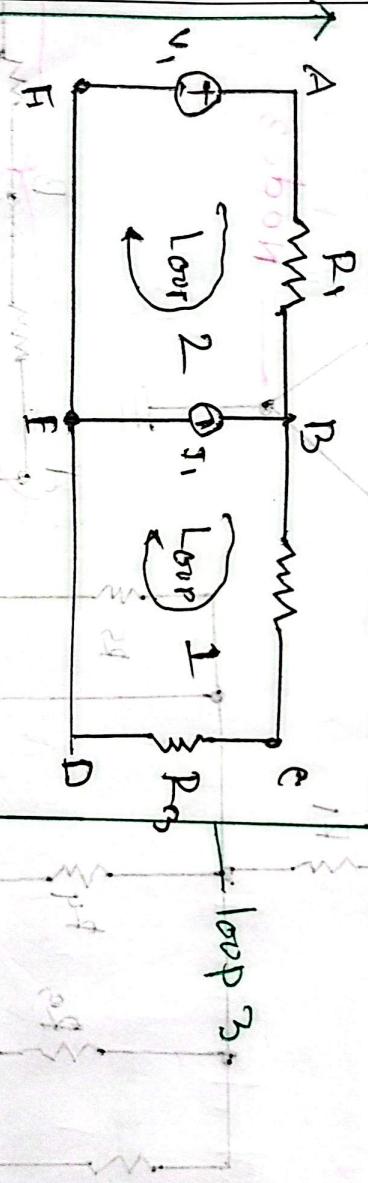

loop 1

loop 2

loop 3

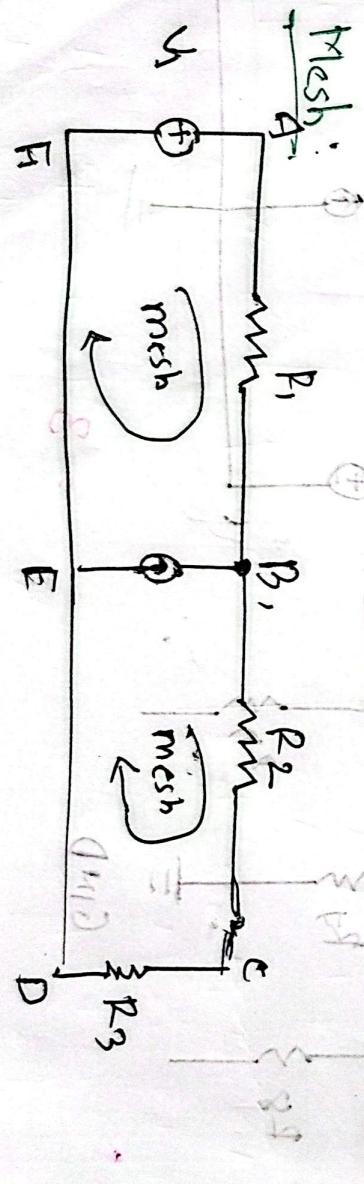

mesh 1

mesh 2

mesh 3

A mesh is a loop do not contain any other loops within it.

Kirchhoff Voltage Law (KVL)

Date:

Kirchhoff Current Law (KCL)

Date:

$KCL = \text{Kirchhoff current law}$ states that algebraic sum of currents entering node zero

$$\sum I = 0$$

Entering $\rightarrow +$ positive
leaving $\rightarrow -$ negative

$$IR = I_1 + I_2$$

$$IR = I_1 + I_2 + I_3$$


$$V_1 + V_2 + V_3 + V_4 + V_5 = 0$$

$$i_1 + i_2 + i_3 + i_4 + (-i_5) = 0$$

KVL: closed path all voltage sum = 0

$$\sum V = 0$$

voltage drop \rightarrow voltage gain

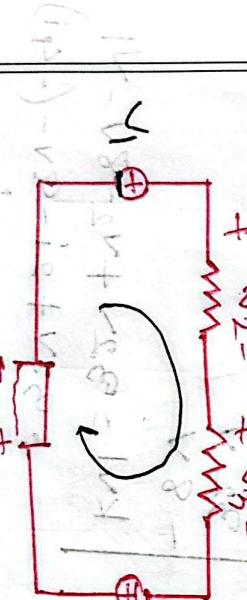

$$V_1 + V_2 + V_3 + V_4 + V_5 = 0$$

$$IR = V - V_{out}$$

$$IR = V_{out} - V$$


$$IR = V - V_{out}$$

$$IR = V_{out} - V$$

(Date) _____ Date: _____
Page No. _____

Find voltage gives current

2.5.

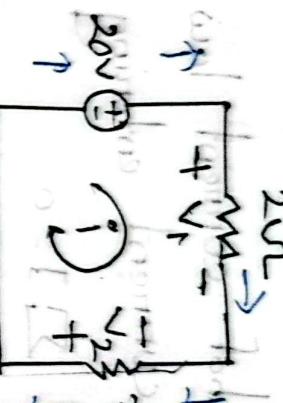

Find Voltage
 V_1 and V_2

Gives $V_1 = 2\text{V}$

$$V_2 = 3(-i)$$

$$= -20 + 2i - (-3i) = 0$$

$$20\sqrt{1+i^2} + 5i = 0 \quad \text{carefully}$$



we know

$$\cancel{R} V = 1\text{A}$$

$$V_1 = 8$$

$$V_2 = 3 \times 4$$

$$= 12$$

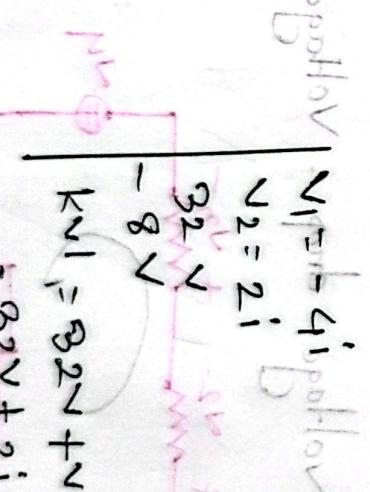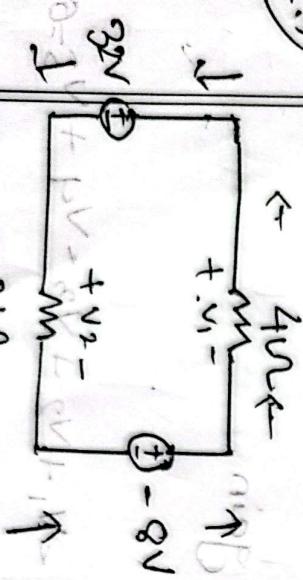

$$V_1 = 4i \text{ volt}$$

$$V_2 = 2i$$

$$32V = 2i$$

$$-8V$$

$$kvl = 32V + V_2 - 8V - V_1$$

$$V_1 = -4x - 4 = 16$$

$$V_2 = -4x 2 = -8$$

$$32V + (-8) - 8V - 16$$

$$32 - 32 = 0$$

Ans correct

$$i = -4$$

Date

$$\text{KVL: } -12V + 4i + 2V_0 - 4 + 6i = 0 \quad \text{ohm's law}$$

$$= -16V + 10i + 2V_0 = 16$$

$$= 10i + 2(-6i) = 16$$

$$= -2i = 16$$



$$\therefore i = -8A$$

$$V_1 = 4i$$

$$V_2 = -6i$$

$$V_0 = (-i) \cdot 2 = -6i$$

$$V_0 = -6(-8) = 48V$$

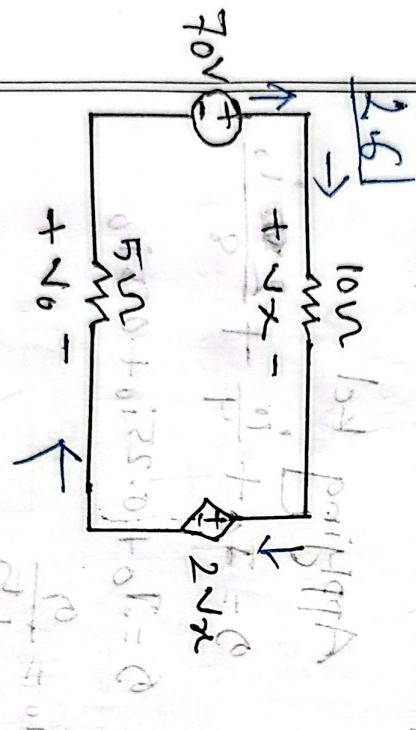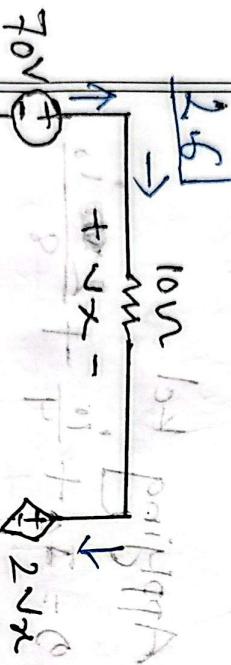

$$-70V + 10i + 2V_0 - (-5i) = 0$$

$$-70V + 10i + (2 \times 10i + 5i) = 0$$

$$\Rightarrow -70V + 35i = 70V$$

$$i = \frac{-70}{35} = 2A$$

$$V_x = 10 \times 2 = 20V$$

$$V_0 = -5 \times 2 = -10V$$

28


Date

$$k_{el} = 0.5 \frac{I_{tot}}{I_n} + \frac{3 - I_0}{\frac{I_n}{6\omega}} = 0$$

$$0.5 \cdot \frac{1}{1} + \frac{3 - I_0}{\frac{1}{6\omega}} \Rightarrow I_0 = 3 + 0.5 I_0$$

$$I_0 = 3 + 0.5 I_0 \Rightarrow I_0 = 6A$$
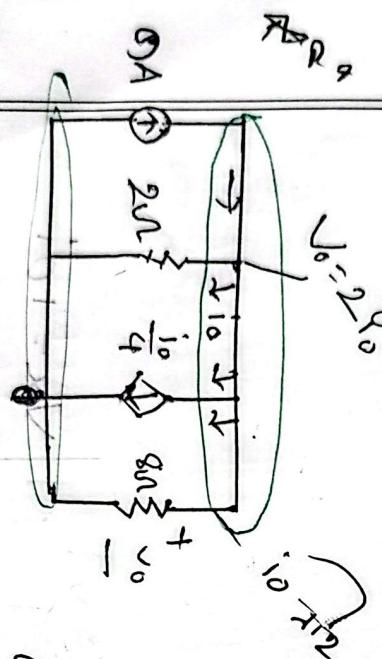
$$V_{SP} = (R + \frac{1}{C}) I_0 = 14 \times 6 = 24V$$



Applying k_{el} law

$$I_0 = \frac{V_0}{10} + \frac{I_0}{4} + \frac{2 - I_0}{2}$$

$$I_0 = I_0 + 0.25 I_0 + 0.25 I_0$$

$$I_0 = \frac{9}{15}$$

$$V_0 = 2 \cdot 6 = 2 \times 6$$

$$= 12 \sqrt{3} \text{ V}$$

$$I_0 = 1.0 \text{ A}$$

$$0 = 1.0(10) + 1.0 + V_{OF} - 1.0 \times 2$$

$$V_{OF} = 1.0 \text{ V}$$


$$V_{OF} = 1.0 \times 0.1 = 0.1 \text{ V}$$

REDMI NOTE 13
SHAKIR HOSSAN


$$10 \Omega = \frac{0.1}{250} = 1$$

Series Resistors and Voltage

Date:

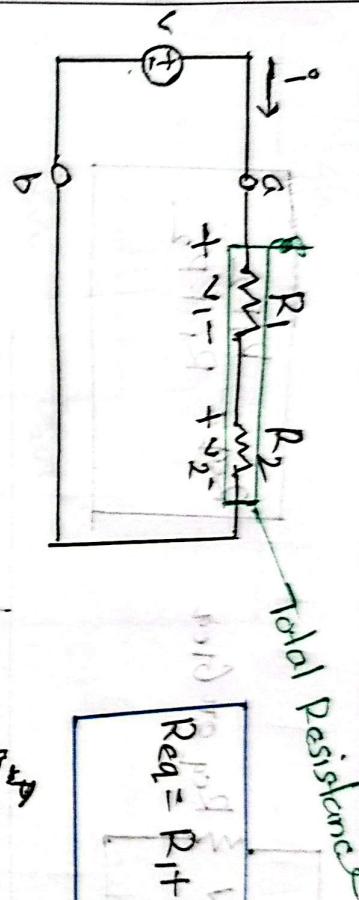
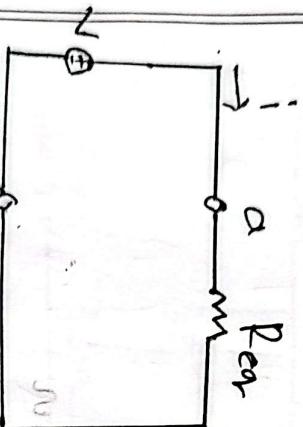
$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{n=1}^N R_n$$




$$\frac{V_1}{R_1} = \frac{V_2}{R_2} = \dots = \frac{V_N}{R_N}$$

Law

True checker not possibl

$$\begin{aligned} V_1 &= V_2 \\ \frac{V_1}{R_1} &= \frac{V_2}{R_2} \\ i_1 &= \frac{V_1}{R_1}, \quad i_2 = \frac{V_2}{R_2} \end{aligned}$$

Parallel Resistor and Current Division

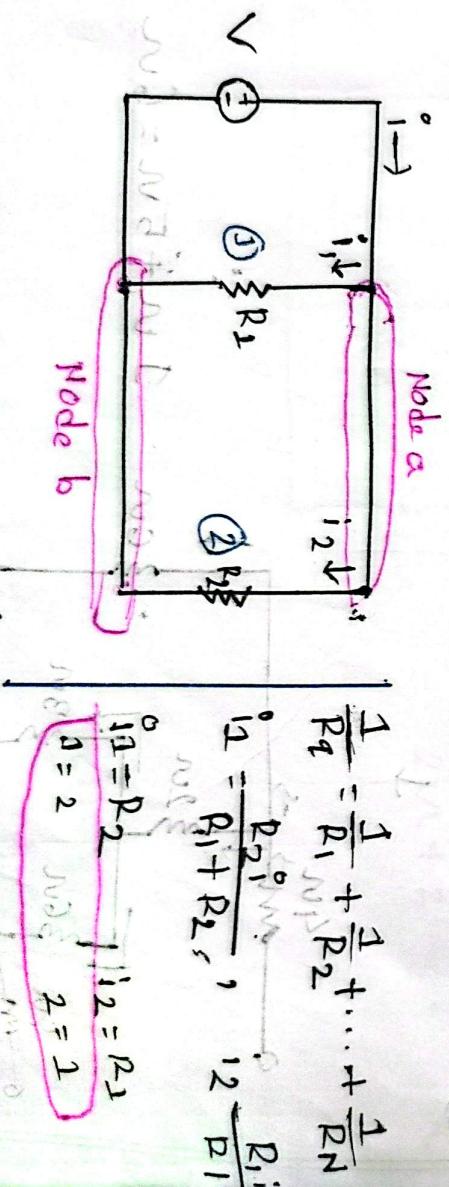


$$\frac{1}{R_q} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

$$I = \frac{R_1}{R_1 + R_2 + \dots + R_N}$$

$$i_1 = \frac{R_2}{R_1 + R_2 + \dots + R_N} I$$

$$i_2 = \frac{R_1}{R_1 + R_2 + \dots + R_N} I$$

Date:
Topic:

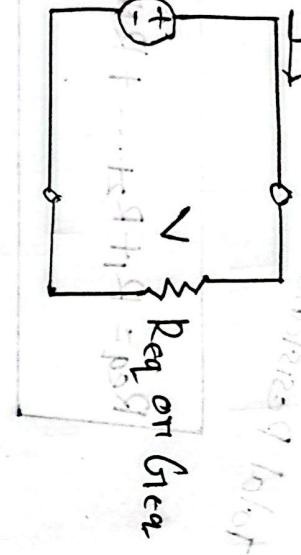

$$R_{\text{eq}} \text{ on Gnd}$$


$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$

$$i_1 + i_2 = i$$

$$i_1 R_1 = i_2 R_2$$

→ True. ok.

Find R_{eq} for the circuit?

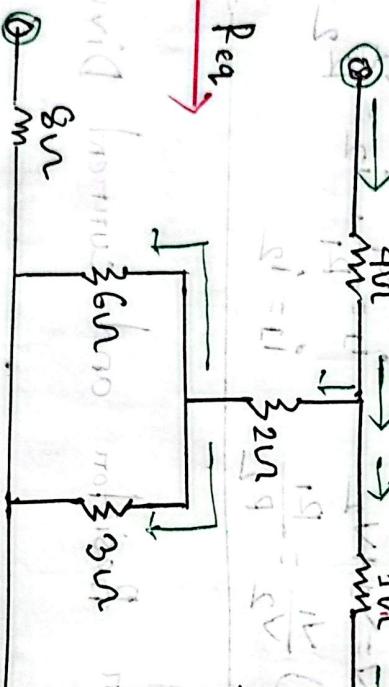


Method 1 using
Muller's
method

$$R_{\text{eq}} = \frac{4 \times 3}{4 + 3} = \frac{12}{7} \Omega$$

$$R_{\text{eq}} = \frac{3 \times 3}{3 + 3} = \frac{9}{6} = \frac{3}{2} \Omega$$


Method 2

$$R_{\text{eq}} = \frac{3}{2} \Omega$$

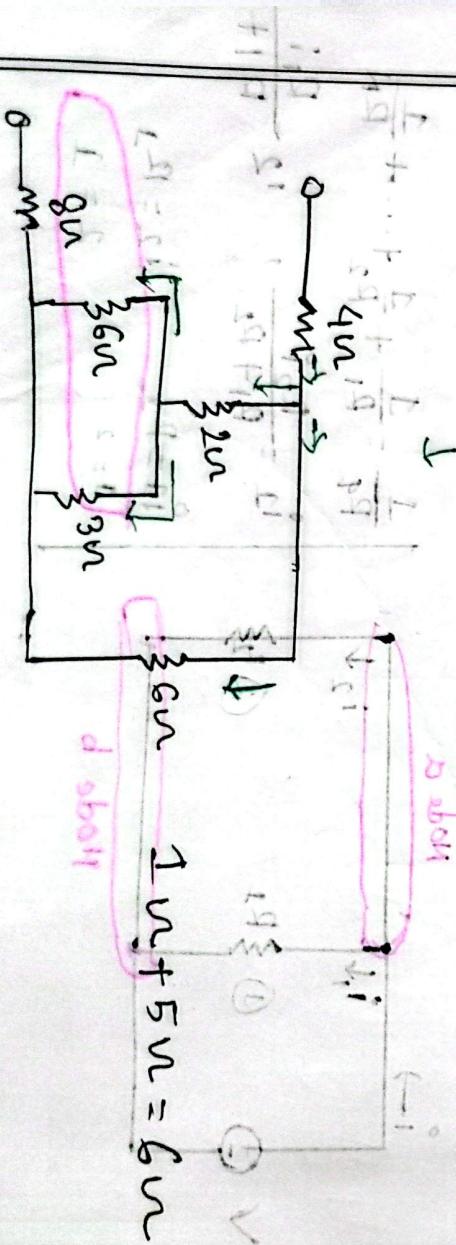


$$1 \text{ m} + 5 \text{ m} = 6 \text{ m}$$


Date:

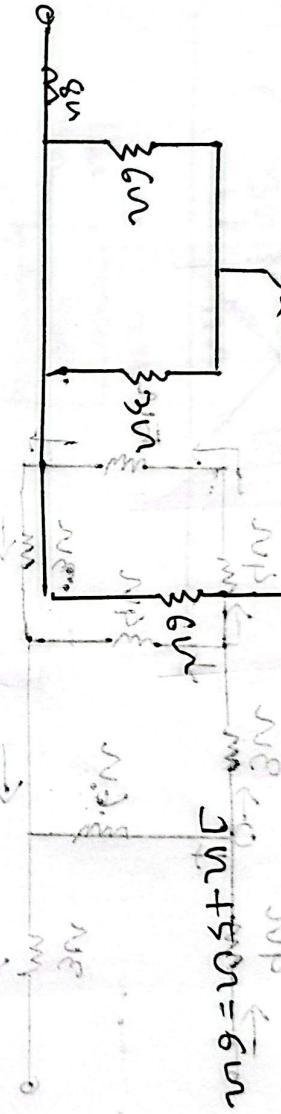
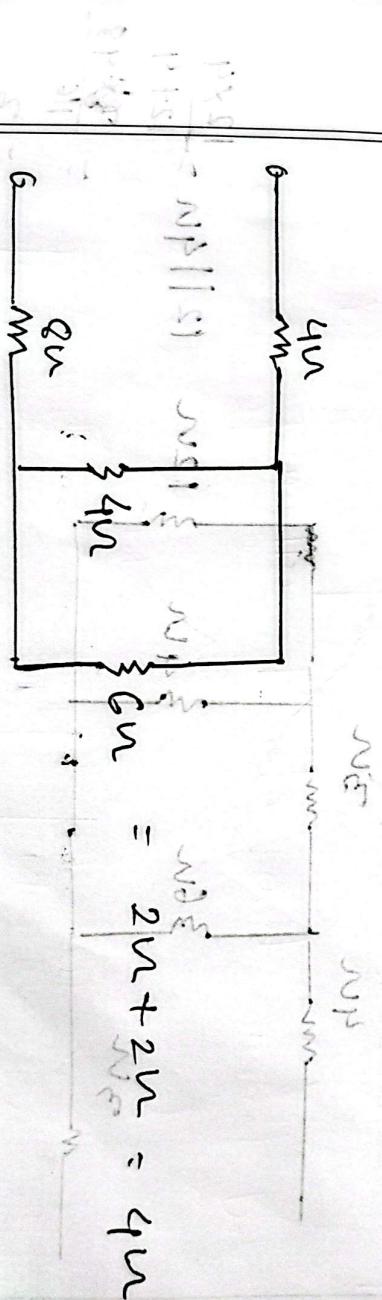
$$G = \frac{1}{R} = \frac{1}{\frac{1}{4} + \frac{1}{6}} = \frac{12}{10} = 1.2 \text{ S}$$
$$E_{equivalent} = G \times R_{parallel} = 1.2 \times 3 = 3.6 \text{ V}$$


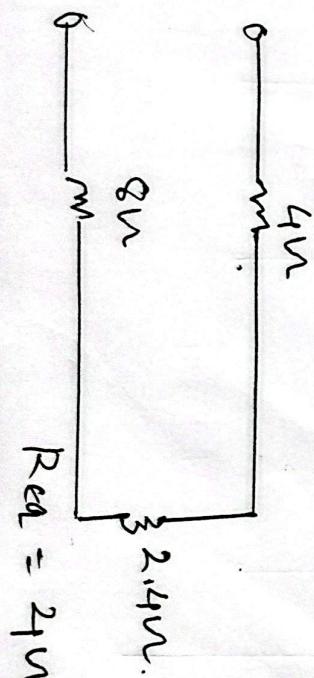
$$\frac{1}{R_{parallel}} = \frac{1}{4} + \frac{1}{6} = \frac{10}{24} = \frac{5}{12} \text{ S}^{-1}$$






REDMI NOTE 13
SHAKIB HOSSAN

$$R_{parallel} = \frac{1}{\frac{5}{12}} = 2.4 \Omega$$

$$\frac{1}{R_{parallel}} = \frac{1}{4} + \frac{1}{6} = \frac{10}{24} = \frac{5}{12} \text{ S}^{-1}$$


Date ::

2.9 practice problem find Req?

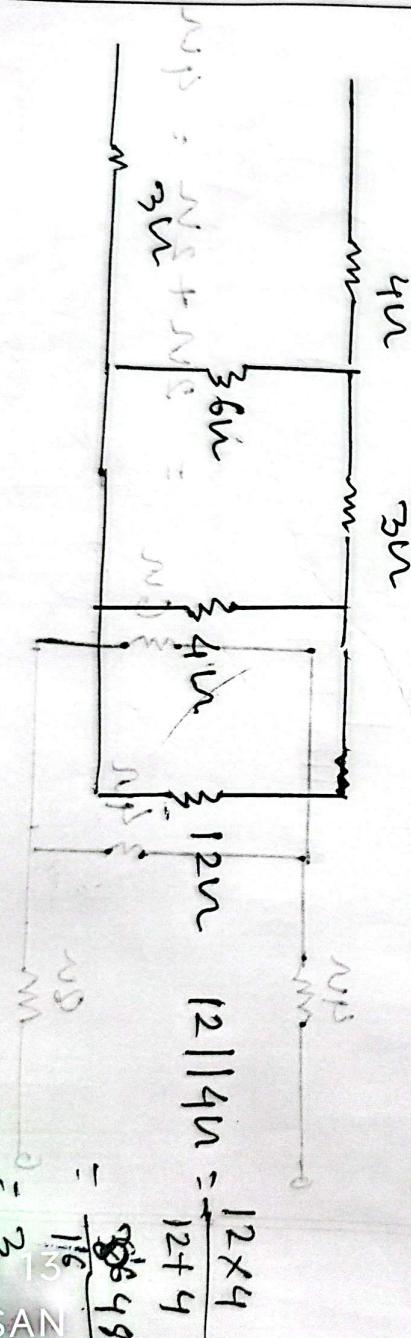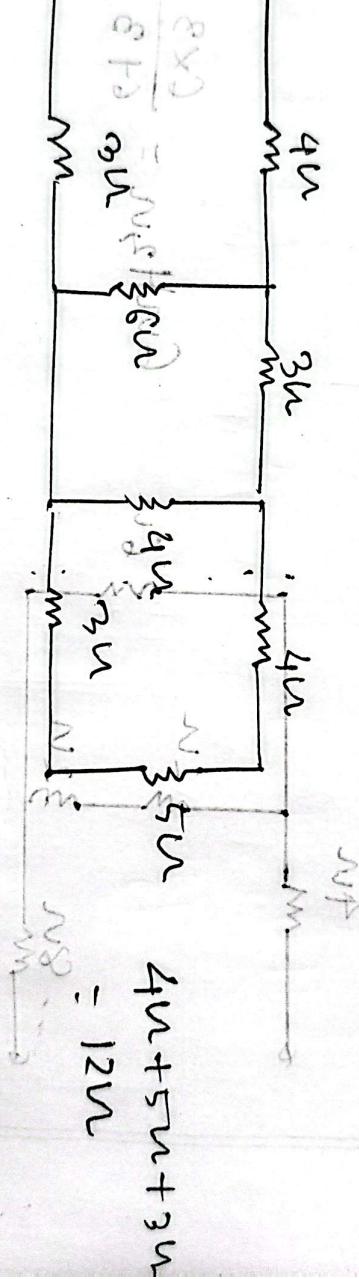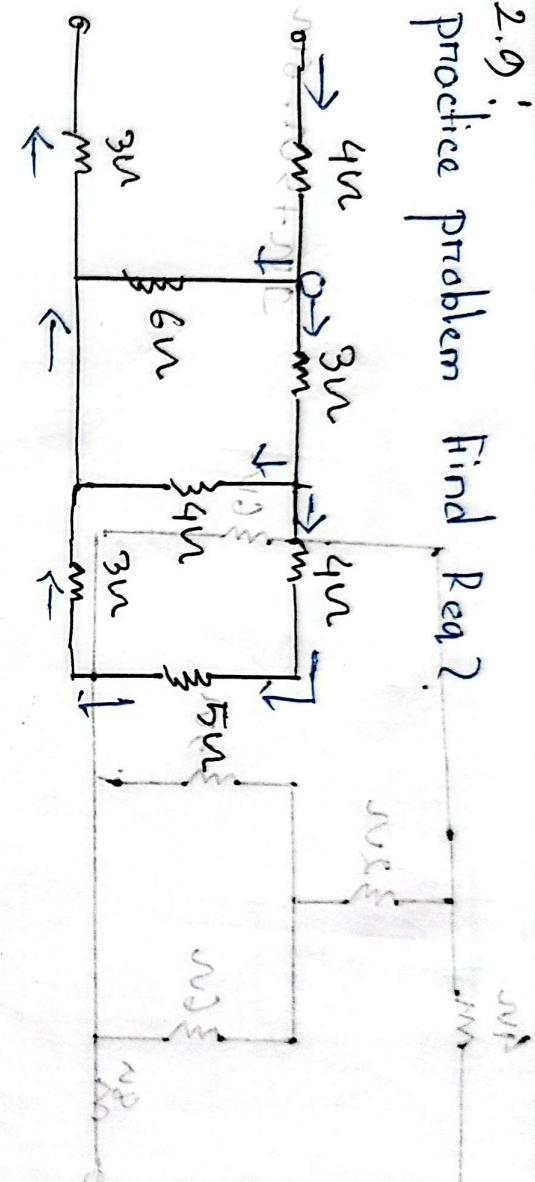

$$W_1^2 = \frac{3 \times 12}{6+4} = 5.4 \text{ m}^3/\text{s}$$
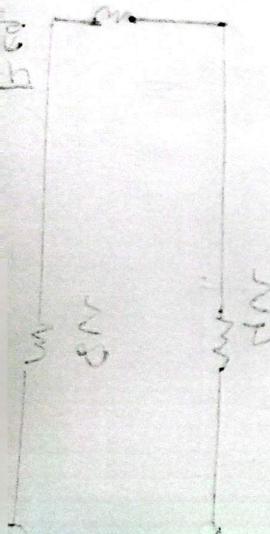
$$W_2^2 = \frac{3 \times 12}{6+4} = 5.4 \text{ m}^3/\text{s}$$




REDMI NOTE 13
SHAKIB HOSSAN

1 Delta to wye conversion

Date

Connec~~Y~~

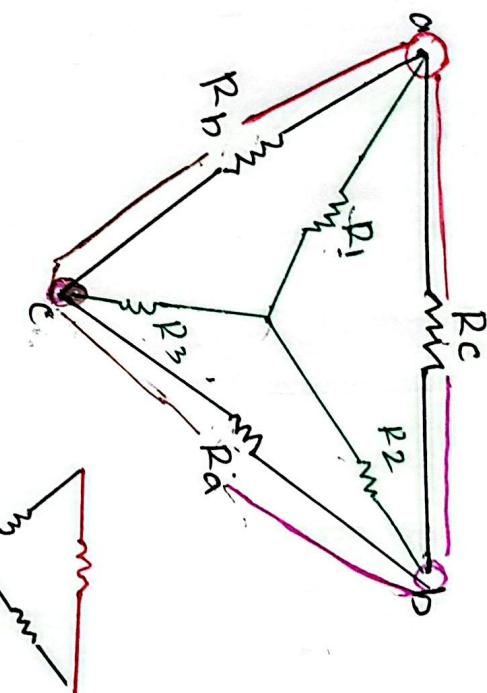

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$



$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

to Delta conversion

carefully

opposite line

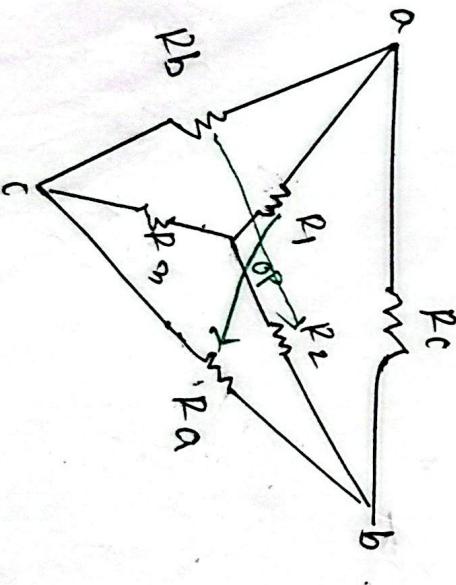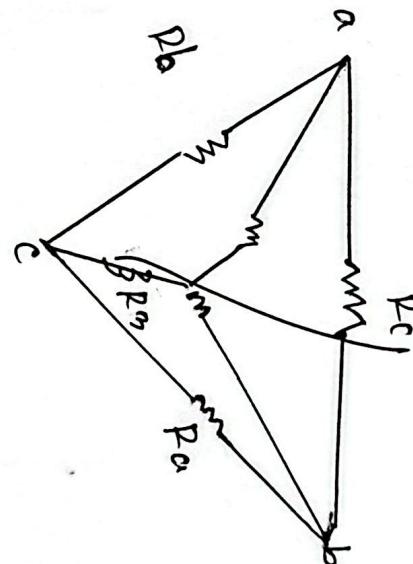like $R_b \rightarrow R_1$, R_3 connected
but opposite = R_2 .



$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

Date

$\Delta = \text{Resistance Delta}$

$\Delta = Y$
Short tricks.

$\Delta = Y$
Dell to P

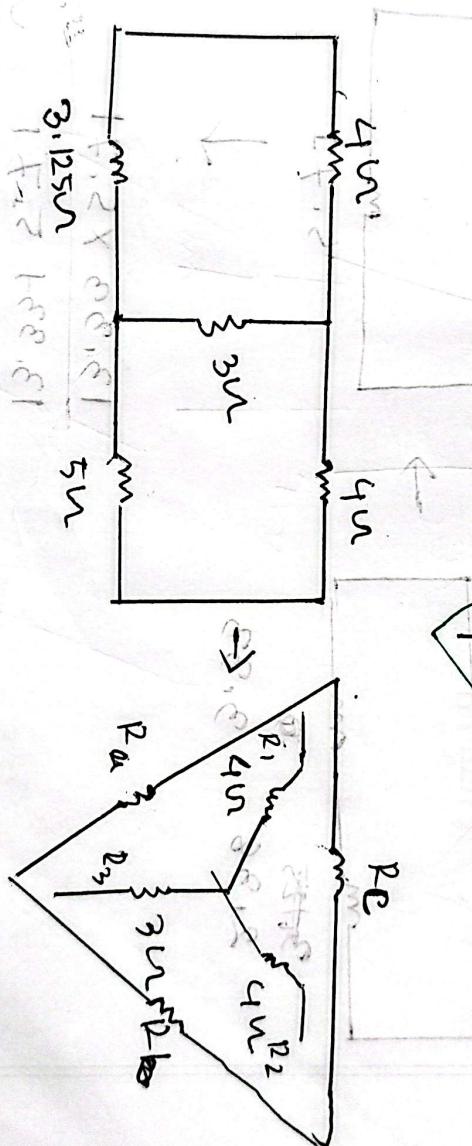

$$R_a = \frac{(4 \times 4) + (4 \times 3) + (3 \times 4)}{3} = \frac{40}{3} \Omega = 13.33\Omega$$

$$R_b = \frac{(4 \times 4) + (4 \times 3) + (3 \times 4)}{4} = \frac{40}{4} \Omega = 10\Omega$$

$$R_c = \frac{40}{4} = 10\Omega$$


Date

Transformation Source

Voltage to Current

Ques 1

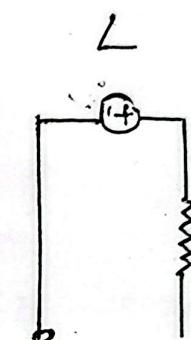Condition :- Voltage \rightarrow Series "P.T. - Transformer"




$$I_o = \frac{V_s}{R} = \text{--- same ---}$$

Condition :- Same - কার্য পরал্লেল - ২৮০ কার্য পরামর্শ

Current Source to Voltage

Condition :- কার্য সিরিজ - কার্য পরামর্শ

$$V_s = I R$$

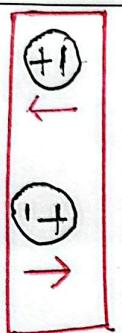

$$V_s = \frac{R}{R_1 + R_2} \times V$$

$V_o > D^o$ ider Rules . $I_o = \frac{R_2}{R_1 + R_2} \times I$ — Total current

$$V_o = I_o R$$


Dependent = loop .

$$I_o =$$



Date :

B.P.

[4.6]

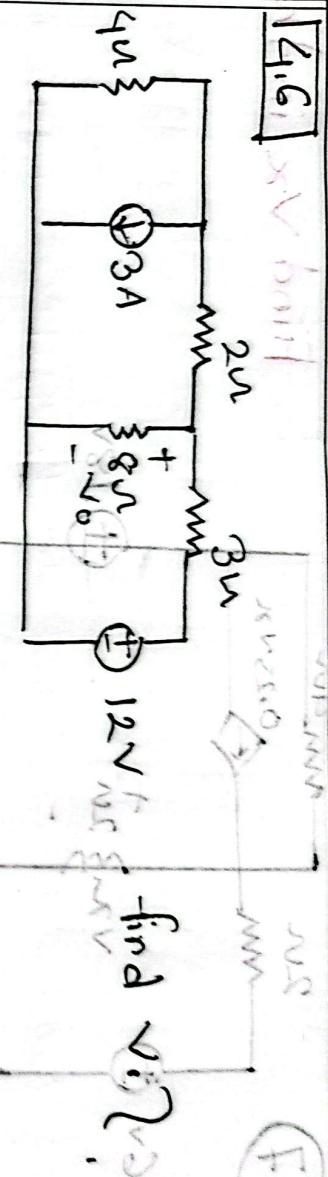


F.P.

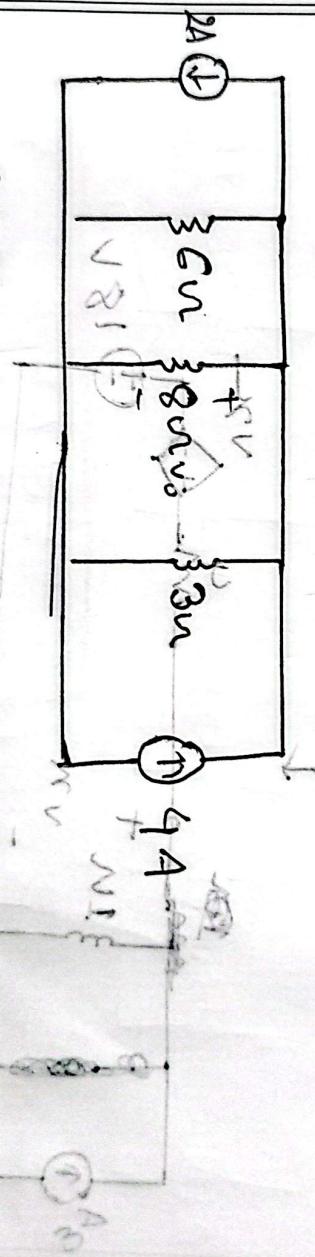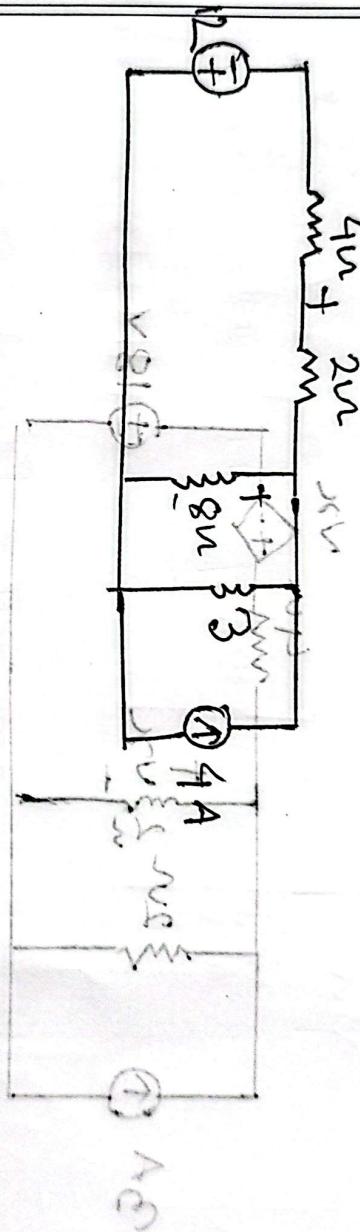

$$G \parallel 3 = 2$$

$$14 - 2x = 2x$$

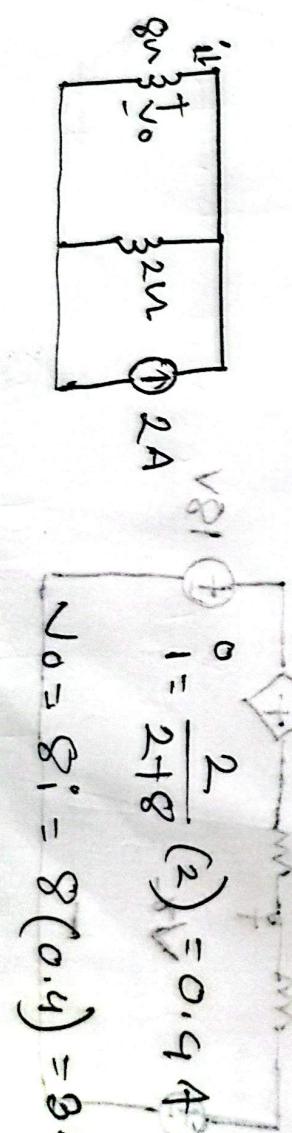

$$V_o = 8i = 8(0.4) = 3.2$$

Hence $V_o = 3.2V$

REDM NOTE 135
SHAKIB HOSSAN

1st year
Electrical
Engineering

Capacitor

Date

$$i(t) = C \frac{dV}{dt} \quad V(t)$$

$$v = \frac{1}{C} \int_{t_0}^t i(t) dt + V_0$$

$$P(t) = CV(t) - \frac{dV}{dt}$$

$$\omega(t) = \frac{1}{2} CV^2(t) - \frac{1}{2} CV^2(-\infty)$$

$$V_1 = \frac{q_1}{C_1}$$

$$q_1 = C_1 V_1$$

$$V_1 = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots}$$

$$\frac{b-b}{b+b} = \frac{1}{2}$$

$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$

capacitor \leftrightarrow resistance

$$MR = 10^3$$

current follow opposite direction

voltage across phasor

Voltages

$$(t) = V_0 + \frac{1}{C_1} \int_{t_0}^t i(t) dt$$

Inductor

Date :

$$\nabla(t) = L \frac{di}{dt}(t) \rightarrow \text{Voltage - Inductance}$$

$$\frac{1}{L} \int_{t_0}^t \nabla(v) dv + v_i(t_0)$$

$$P(t) = L i(t) \frac{di}{dt}(t)$$

$$\omega(t) = \frac{1}{2} L i^2(t) - \frac{1}{2} L i_0^2$$

$$\nabla L = \frac{\text{Total Current} \times R_{\text{total}}}{\text{Total Resistance}}$$

$$\frac{d}{dt}(e^{at})$$

$\Rightarrow e^{at}$

Lesson → Remember it

$\frac{3}{4}$ = Supposition theorem, Date.....

$$VDR = \frac{\text{Main Resistance}}{\cancel{\text{Main}} + \text{opposite R}} \times \text{Total Voltage}$$

$$CDR = \frac{\text{opposite Resistance}}{\text{Total current}} \times 100$$

Dependent |

 mesh analysis, otherwise CDR+VDR

$$I = \frac{V}{R}, \quad V = IR,$$

ପ୍ରମାଣ-କାନ୍ତି-ବିଜ୍ଞାନ-ଶାସନ-କାନ୍ତି-
ପ୍ରମାଣ-କାନ୍ତି-ବିଜ୍ଞାନ-ଶାସନ-କାନ୍ତି-
ପ୍ରମାଣ-କାନ୍ତି-ବିଜ୍ଞାନ-ଶାସନ-କାନ୍ତି-

2.2 (ii) I₂ current formation → जला ताप - नियन्त्रण करने का लिए - loop adjust करो।

A hand-drawn diagram of a magnetic core. It consists of two vertical rectangular legs at the top and a single vertical rectangular leg in the center. A horizontal rectangular leg connects the two vertical legs. Inside the central vertical leg, there is a circular arrow pointing clockwise, representing the direction of current flow.


جی ۱۷

Superposition \Rightarrow sum of \vec{E} by all
just independent source,

Important,

Date :.....

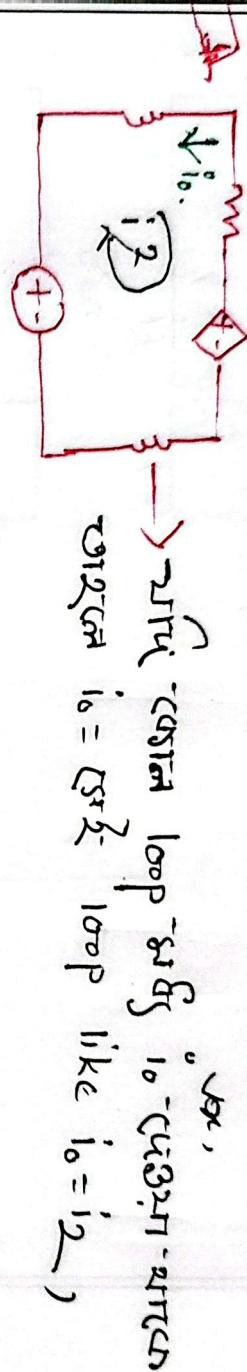Direction - क्रियालय - दण्डा $\uparrow G = -$,
current Source, $\uparrow \text{C} = +$



+ स्टेचर्स - स्टेचर्स - अलग - न्यून - न्यून के तथा तर्क के
Dependent Source - न्यून के तर्क
CDR - $v_{DR} = 2.15 \text{ V}$